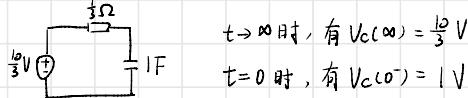


Chapter 3 3.4

对于 ODE: $K = \frac{dy}{dt} + ay(t)$, 对于 $t > 0$, 有 $y(t) = y_p(t) + y_h(t) = B + Ae^{-at} = \frac{K}{a} + (y(0^+) - \frac{K}{a})e^{-at}$

例: $V_C(0^-) = 1V$, 计算 $V_C(t)$



$t \rightarrow \infty$ 时, 有 $V_C(\infty) = \frac{10}{3} V$

$t=0$ 时, 有 $V_C(0^-) = 1V$


$$\Rightarrow V_C(t) = \frac{10}{3} - \frac{7}{3} e^{-\frac{t}{1}} [V]$$

Zero-input: 电路没有任何外部驱动信号

Zero-state: 电路初始条件为 0, 仅考虑外部驱动信号

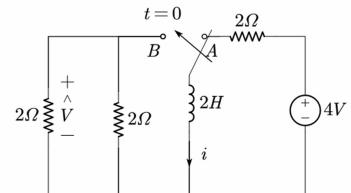例: 圈中开关在 $t=0$ 前在 A, $t=0$ 时切换到 B, 求 $i_{zi}(t)$ 和 $i_{zs}(t)$

$$i(0^-) = 2A \quad i_{zi} = 2e^{-\frac{t}{2}}, \quad i_{zs} = 0$$



First-Order ODE with Time-Varying Input

$$f(t) = \frac{dy}{dt} + ay, \text{ 有 } y_h(t) = Ae^{-at}, \quad y_p \left\{ \begin{array}{l} B \\ Be^{-pt} \\ Bte^{-at} \\ H\cos(\omega t + \phi) \end{array} \right.$$

$$\begin{aligned} f(t) &= K \\ f(t) &= ke^{-pt} \quad (a \neq p) \\ f(t) &= Ke^{-at} \\ f(t) &= K\cos(\omega t + \theta) \end{aligned}$$

例: $\frac{dy}{dt} + y = e^{-2t}$, $y(0^+) = 1$, 计算 $y_{zs}(t)$, $y_{zi}(t)$, $y(t)$

$\frac{dy}{dt} + y = e^{-2t}$, 先求通解 $y' + y = 0 \Leftrightarrow \lambda + 1 = 0 \Rightarrow y_h = Ae^{-t}$, 且特解中, $-2 \neq -1$, $\therefore y_p = Be^{-2t}$

$$\therefore y = Ae^{-t} + Be^{-2t} \quad \left\{ \begin{array}{l} -Ae^{-t} - 2Be^{-2t} + Ae^{-t} + Be^{-2t} = e^{-2t} \\ A + B = 1 \end{array} \right. \Rightarrow \left\{ \begin{array}{l} A = 2 \\ B = -1 \end{array} \right.$$

$$\Rightarrow y = 2e^{-t} - Be^{-2t}$$

$$\text{例: } \frac{dy}{dt} + y = \cos(t)$$

$$y' + y = 0 \Rightarrow y_h = Ae^{-t}, \quad y_p = B\cos t + C\sin t \quad \text{fit into ODE: } -Bs\sin t + Cs\cos t + B\cos t + C\sin t$$

$$\Rightarrow \begin{cases} -B + C = 0 \\ B + C = 1 \end{cases} \Rightarrow \begin{cases} B = \frac{1}{2} \\ C = \frac{1}{2} \end{cases} \quad \because y_p = \frac{1}{2}(\cos t + \sin t), \text{ fit } \lambda y(0) = 1, A = \frac{1}{2}$$

$$c_1 y = \frac{1}{2} e^{-t} + \frac{1}{2} \cos t + \frac{1}{2} \sin t$$


对于零输入，有 $y' + y = 0 \Rightarrow y_{zi} = e^{-t}$

对于零状态，有 $y_{zs} = \frac{1}{2} \cos t + \frac{1}{2} \sin t$ ，且因不满足零状态 $y(0)=0$ ，需加入零状态 $Ce^{-t} \Rightarrow C = -\frac{1}{2}$
 $\Rightarrow y_{zs} = \frac{1}{2} \cos t + \frac{1}{2} \sin t - \frac{1}{2} e^{-t}$

Transient State and Steady State

① 过渡状态 ② 稳态

N -th Order LTI system

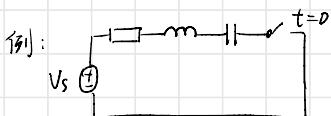

$$V_s = V_R + V_L + V_C \quad , \quad V_R = iR \quad , \quad V_L = L \frac{di}{dt} \quad , \quad V_C = V_0$$

$$\text{又 } \because i_L = C \frac{dV_C}{dt} \Rightarrow V_R = RC \frac{dV_C}{dt}, \quad V_C = L \frac{d}{dt}(C \frac{dV_C}{dt}) = LC \frac{d^2V_C}{dt^2}$$

$$\Rightarrow \frac{d^2V_C}{dt^2} + \frac{R}{L} \frac{dV_C}{dt} + \frac{1}{LC} V_C = \frac{1}{LC} V_S(t)$$

$$\text{代入 } R=0, L=C=1, V_S=0 \Rightarrow \frac{d^2 V_C}{dt^2} + V_C = 0$$

Phasor

$$f(t) = A \cos(\omega t + \theta) = \operatorname{Re} \{ A e^{j(\omega t + \theta)} \} = \operatorname{Re} \{ A e^{j\theta} e^{j\omega t} \} = \operatorname{Re} \{ F e^{j\omega t} \}$$

$$\Leftrightarrow F = A e^{j\theta} = |\underline{A}| \angle \theta \rightarrow \text{magnitude phase}$$

例：将下列函数写成 phasor 形式：

$$\textcircled{1} f_1(t) = \cos(10t)$$

$$f_1(t) = \operatorname{Re} \{ A e^{j(10t + 0)} \} = \operatorname{Re} \{ A e^{j0} \cdot e^{j10t} \} = \operatorname{Re} \{ e^{j10t} \} \Leftrightarrow F = 1$$

$$\textcircled{2} f_2 = \frac{1}{2} \cos(10t + \frac{\pi}{4}) = \operatorname{Re} \{ \frac{1}{2} e^{j\frac{\pi}{4}} \cdot e^{j10t} \} \Leftrightarrow F = \frac{1}{2} e^{j\frac{\pi}{4}}$$

$$\textcircled{3} f_3 = \sqrt{3} \sin(10t) = \sqrt{3} \cos(10t - \frac{\pi}{2}) = \operatorname{Re} \{ \sqrt{3} e^{j-\frac{\pi}{2}} \cdot e^{j10t} \} \Leftrightarrow F = \sqrt{3} e^{j-\frac{\pi}{2}} = -j\sqrt{3}$$

Superposition Principle for Phasors

$$f_1(t) = \operatorname{Re} \{ F_1 e^{j\omega t} \} \Rightarrow F_1$$

$$f_2(t) = \operatorname{Re} \{ F_2 e^{j\omega t} \} \Rightarrow F_2$$

$$\left. \begin{array}{l} f_3(t) = k_1 f_1(t) + k_2 f_2(t) \\ \Rightarrow F_3 = k_1 F_1 + k_2 F_2 \end{array} \right\}$$

$$\begin{aligned} \text{If: } & \begin{array}{c} \xrightarrow{i_1 = -3 \cos(3t)} \\ \downarrow i_3 \\ \xleftarrow{i_2 = 4 \sin(3t)} \end{array} & \text{先写成 phasor 形式: } I_1 = -3, I_2 = 4e^{j-\frac{\pi}{2}} = -4j \\ & I_3 = I_1 + I_2 = -3 - 4j = A e^{j\theta} & \Rightarrow \begin{cases} A = 5 \\ \theta = \pi + \arctan \frac{4}{3} \end{cases} \end{aligned}$$

$$\Rightarrow i_3(t) = 5 \cos(3t - \pi - \arctan(\frac{4}{3})) [A]$$

Derivative Principle

$$f(t) = \operatorname{Re} \{ F e^{j\omega t} \}, g(t) = \frac{d f(t)}{dt} = \operatorname{Re} \{ \underline{F} \cdot j\omega e^{j\omega t} \}$$

$$n\text{-th order: } \frac{d^n f}{dt^n} \rightarrow (j\omega)^n F$$

$$例: f(t) = 3 \cos(2t + \frac{\pi}{4}), \text{求 } f'(t).$$

$$F = 3e^{\frac{\pi i}{4}} = 3(\cos \frac{\pi}{4} + j \sin \frac{\pi}{4}) = \frac{3}{2}\sqrt{2} + j\frac{3}{2}\sqrt{2}, \quad F' = j\omega F = j2(\frac{3}{2}\sqrt{2} + j\frac{3}{2}\sqrt{2}) = -3\sqrt{2} + j3\sqrt{2}$$

$$A = \sqrt{(3\sqrt{2})^2 + (3\sqrt{2})^2} = 6, \quad \theta = \frac{3}{4}\pi, \quad \therefore f'(t) = 6 \cos(2t + \frac{3}{4}\pi)$$

例: determine the steady state solution: $\frac{d^2y}{dt^2} + 2\frac{dy}{dt} + y = -5 \sin(2t)$

$$(j\omega)^2 Y + 2j\omega Y + Y = -5e^{-j\frac{\pi}{2}} \Leftrightarrow -4Y + 4jY + Y = 5j \Leftrightarrow Y = \frac{5j}{-3+j4}$$

$$\Rightarrow Y = \frac{1}{5}j(-3-j4) = \frac{-4+3j}{5}, \quad A=1, \quad \theta = \pi - \arctan \frac{3}{4}$$

$$\Rightarrow y(t) = \cos(2t - \pi + \arctan \frac{3}{4})$$

例: $\dot{i}_s = \frac{1}{j} \int_{ss}^t i_s(t)$

$$\begin{aligned} & \text{Circuit diagram: } \begin{array}{c} 1\Omega \\ \parallel \\ 3\Omega \\ \parallel \\ 1H \end{array} \stackrel{j\cos(3t)V}{=} \frac{1}{j}F \quad Z_L = j\omega L = j3, \quad Z_C = -j\frac{1}{\omega C} = -j3 \end{aligned}$$


$$\begin{array}{c} jA \\ \oplus \\ 1\Omega \\ \parallel \\ 3\Omega \\ \parallel \\ j3 \end{array} \stackrel{= -3j}{=}$$

$$\begin{aligned} \frac{1}{Z_{tot}} &= \frac{1}{1} + \frac{1}{3+j3} + \frac{1}{-3j} \\ &= \frac{3(1+j) + 1 + j(1+j)}{3(1+j)} = \frac{3+4j}{3(1+j)} \end{aligned}$$

$$Z_{tot} = \frac{3+3j}{3+4j} = \frac{1}{25}(3+3j)(3-4j) = \frac{1}{25}(21-3j) \Rightarrow I = \frac{2j}{-3j} \cdot 5 = 5 \cdot \frac{1}{25}(21-3j) \cdot -\frac{1}{-3j} = \frac{1}{5}(1+7j)$$

$$A = \frac{\sqrt{5}}{5} = \sqrt{2}, \quad \theta = \arctan 7, \quad i_{ss} = \sqrt{2} \cos(3t + \arctan 7)$$

例: determine V_T, I_N, Z_T

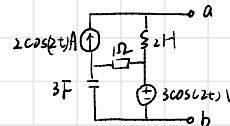

$$Z_C = -j\frac{1}{\omega C} = -j\frac{1}{2}, \quad Z_L = j\omega L = j4$$

For V_T , first let voltage source being shorted. $V_1 = 2 \times j4 = j8 [V]$

then let current source being opened $V_2 = 3[V]$

$$\Rightarrow V_T = 3+j8$$

$$Z_T: \text{Use a test signal } I = 1[A], \quad V = 1 \times j4 = j4 \quad \therefore R_T = j4 \quad \Rightarrow I_N = \frac{3+j8}{4j} [A]$$

Average Power


$$P_R = \frac{1}{2} |I|^2 R = \frac{1}{2} \frac{|V|^2}{R}$$

$$P_L = P_C = 0$$

Available Power: Maximum (average) absorbed power by the load.

$$P_a = \frac{1}{8} \frac{|V|^2}{R_T}$$

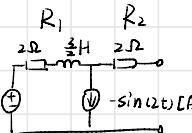例: Determine the available average absorbed power $2\cos(2t)V$



$$\Rightarrow V = 2, I = -e^{-j\frac{\pi}{2}} = j A$$

① The current source opened

② The voltage source shorted $\Rightarrow V_T$, Then use test signal to get Z_T

$$P_a = \frac{1}{8} \frac{|V_T|^2}{R_T} \rightarrow \text{here } R_T \text{ is the real part of } Z_T$$


Resonance $\omega_0 = \frac{1}{\sqrt{LC}}$

$$\text{串联 LC 电路中, } \frac{V_c}{V_L} = \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega L}} = \frac{1}{1-\omega^2 LC}, \text{ as } \omega \rightarrow \omega_0, \frac{V_c}{V_L} \rightarrow \infty$$

所以, 加入阻尼 R ,

$$\text{并联 LC 电路中, } Z = \frac{1}{\omega L - \omega C} - \frac{j\omega L}{1-\omega^2 LC} \quad \text{as } \omega \rightarrow \omega_0, Z \rightarrow \infty$$

Chapter 5

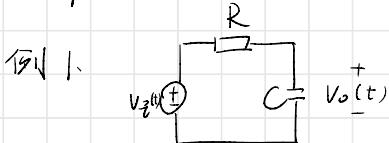

令 $V_i(t) = A \cos(2t + \theta)$, 计算 $V_o(t)$

$$Z_C = -j \frac{1}{\omega C} = -j \frac{1}{2C} \quad V_o = \frac{-j \frac{1}{2C}}{-j \frac{1}{2C} + R} V_i = \frac{1}{1 + 2RC} V_i \quad V_i = \frac{|V_s| e^{j \angle V_i}}{|1 + 2RC|^2 e^{j \arctan(2RC)}}$$


$$\Rightarrow V_o = \frac{A}{|1 + 2RC|^2} e^{j \angle [V_i - \arctan(2RC)]} = \frac{A}{|1 + 2RC|} \cos(\omega t + \phi_i - \arctan(2RC))$$

在这题中, 如果改变输入电压 V_i 的频率, 输出函数也会有相应改变

为了描述输入频率对输出的影响, 引入 $H(\omega)$ 次, 使得 $V_o = V_i H(\omega)$


展开后式子可写为 $V_o = |V_i| |H(\omega)| e^{j(\angle V_i + \angle H(\omega))} = |V_i| |H(\omega)| \cos(\omega t + \angle V_i + \angle H(\omega))$

例:

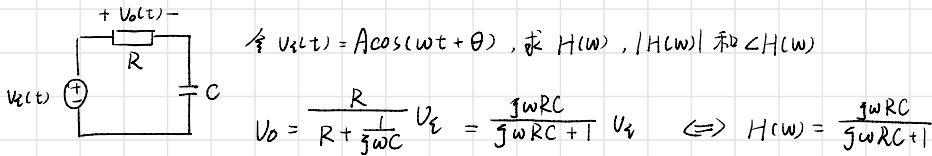


$$V_o = \frac{R}{R + j \frac{1}{\omega C}} V_i = \frac{j \omega RC}{j \omega RC + 1} V_i \Leftrightarrow H(\omega) = \frac{j \omega RC}{j \omega RC + 1}$$

$$|H(\omega)| = \frac{|\omega RC|}{\sqrt{1 + (\omega RC)^2}}, \quad H(\omega) = \frac{j \omega RC (1 - j \omega RC)}{1 + \omega^2 R^2 C^2} = \frac{1}{1 + \omega^2 R^2 C^2} (\omega^2 R^2 C^2 + j \omega RC) \Rightarrow \angle H(\omega) = \arctan \frac{\omega RC}{\omega RC}$$

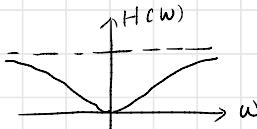

不难发现, 这是一个高通滤波器


例:

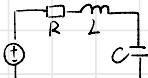

对输出电流 $i(t)$, 求 $H(\omega)$, $|H(\omega)|$, $\angle H(\omega)$

与前例不同的是, 前例是 $H(\omega) = \frac{V_o}{V_i}$, 本例则是 $H(\omega) = \frac{i_o}{V_i}$, 计算的实际是电路的导纳值

$$H(\omega) = \frac{1}{R + j \omega L + j \frac{1}{\omega C}} = \frac{j \omega C}{1 + j \omega RC - \omega^2 LC}, \quad |H(\omega)| = \frac{1}{\sqrt{(1 - \omega^2 LC)^2 + (\omega RC)^2}}$$

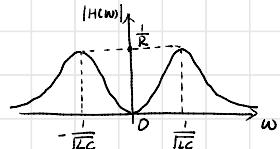

实值 LTI 系统频率响应性质

① 共轭对称 $H(-\omega) = H^*(\omega)$

② 幅度响应为偶函数 $|H(-\omega)| = |H(\omega)|$

③ 相位响应为奇函数 $\angle H(-\omega) = -\angle H(\omega)$

④ 直流响应为实数 $H(0) = H^*(0)$

⑤ 对 $e^{j\omega t}$ 的稳态响应 $e^{j\omega t} \xrightarrow{\text{LTI}} H(\omega) e^{j\omega t}$

Multiple frequencies

$$f(t) = \sum_n c_n \cos(\omega_n t + \theta_n) + \sum_k b_k \sin(\omega_k t + \psi_k) + \sum_m F_m e^{j\omega_m t}$$

$$\begin{aligned} y(t) = & \sum_n c_n |H(\omega_n)| \cos(\omega_n t + \theta_n + \angle H(\omega_n)) + \sum_k b_k |H(\omega_k)| \sin(\omega_k t + \psi_k + \angle H(\omega_k)) \\ & + \sum_m F_m H(\omega_m) e^{j\omega_m t} \end{aligned}$$

Decibel Amplitude Response

$$|H(\omega)|_{dB} = 20 \log_{10}(|H(\omega)|^2) = 20 \log_{10} |H(\omega)|$$

Chapter 6

什么时候若干信号的和信号仍是周期信号？频率比必须是有理数

Exponential Fourier Series

$$f(t) = \sum_{n=-\infty}^{\infty} F_n e^{jn\omega_0 t}$$

例：计算 $f(t) = \cos(t)$ 的 exponential Fourier series

$$f(t) = \sum_{n=-\infty}^{\infty} F_n e^{jn\omega_0 t}, \quad \omega_0 = 1 \text{ rad/s}, \quad \text{已知 } \cos(t) = \frac{e^{jt} + e^{-jt}}{2}$$

$$\therefore F_0 = 0, \quad F_1 = F_{-1} = \frac{1}{2}$$

$$F_n = \frac{1}{T} \int_T f(t) e^{-j n \omega_0 t} dt \quad \text{@@}$$

例： $f(t) = \begin{cases} 1 & t \in [0, 1] \\ 0 & t \in [1, 2] \end{cases}, \quad T = 2s$, 计算 $f(t)$ 的 exponential Fourier series

$$F_n = \frac{1}{T} \int_T f(t) e^{-j n \omega_0 t} dt = \frac{1}{2} \left[\int_0^1 e^{-j n \pi t} dt + \int_1^2 0 e^{-j n \pi t} dt \right] = \frac{1}{2} \cdot \frac{1}{-j n \pi} e^{-j n \pi t} \Big|_0^1$$

$$= -\frac{1}{2 j n \pi} [e^{-j n \pi} - 1] \quad \text{for } n = \begin{cases} 2k, & F_n = 0 \quad (e^{-j 2k \pi} = \cos(-2\pi) + j \sin(-2\pi) = 1) \\ 2k+1, & F_n = \frac{1}{j n \pi} \end{cases}$$

$$\Rightarrow f(t) = \frac{1}{2} + \sum_{n=1, \text{ odd } n}^{\infty} \frac{1}{j n \pi} e^{j n \pi t}$$

Fourier Series Forms

$$\text{Exponential: } f(t) = \sum_{n=-\infty}^{\infty} F_n e^{jn\omega_0 t}$$

$$\text{Trigonometric: } f(t) = \frac{a_0}{2} + \sum_{n=1}^{\infty} (a_n \cos(n\omega_0 t) + b_n \sin(n\omega_0 t))$$

$$a_0 = 2F_0$$

$$a_n = F_n + F_{-n}$$

$$b_n = j(F_n - F_{-n})$$

$$F_0 = \frac{a_0}{2}$$

$$F_n = \frac{a_n - j b_n}{2}$$

$$F_{-n} = \frac{a_n + j b_n}{2}$$

欧拉公式

$$\text{Compact form: } f(t) = \frac{C_0}{2} + \sum_{n=1}^{\infty} C_n \cos(n\omega_0 t + \theta_n) \quad \text{仅用于实值函数}$$

$$C_0 = 2F_0 \quad C_n = 2|F_n| \quad \theta_n = \angle F_n$$

$$F_n = \frac{C_0}{2} e^{j\theta_n}$$

例：对于 $f(t) = \begin{cases} 1 & t \in [0, 1) \\ 0 & t \in [1, 2) \end{cases} \Rightarrow F_n = \begin{cases} \frac{1}{2} & \text{odd} \\ 0 & \text{even} \end{cases}$, 求 $f(t)$ 的 trigonometric 形式

$$f(t) = \frac{1}{2} + \sum_{\text{odd } n=1}^{\infty} \left(\frac{1}{jn\pi} e^{jn\pi t} - \frac{1}{jn\pi} e^{-jn\pi t} \right) = \frac{1}{2} + \sum_{n=1}^{\infty} \frac{2}{n\pi} \sin(n\pi t)$$

例：同上题，求 $f(t)$ 的 compact form.

$$f(t) = \frac{1}{2} + \sum_{\substack{n=1 \\ \text{odd}}}^{\infty} \frac{2}{n\pi} \cos(n\pi t - \frac{\pi}{2})$$

例： $g(t) = \begin{cases} 2 & t \in [0, 1) \\ 0 & t \in [1, 2) \end{cases}$, 求 $g(t)$ 的 exponential form. scaling property

$$g(t) = 2f(t) = 2 \sum_{n=-\infty}^{\infty} F_n e^{jn\omega_0 t} \Rightarrow G_n = 2F_n$$

例： $h(t) = \begin{cases} 0 & t \in [0, 1) \\ 1 & t \in [1, 2) \end{cases}$, 求 $h(t)$ 的 exponential form

$$h(t) = f(t-t_0) = \sum_{n=-\infty}^{\infty} F_n e^{jn\omega_0(t-t_0)} = \sum_{n=-\infty}^{\infty} F_n e^{-jn\omega_0 t_0} e^{jn\omega_0 t} \Rightarrow H_n = F_n e^{-jn\omega_0 t_0}$$

time-shift property

Addition property

$$x(t) = f(t) + g(t) \Rightarrow X_n = F_n + G_n$$

在 LTI system 中，有 $\begin{cases} e^{jwt} \rightarrow \text{LTI} \rightarrow H(w)e^{jwt} \\ \cos(\omega_0 t + \theta) \rightarrow \text{LTI} \rightarrow |H(w)| \cos(\omega_0 t + \theta + \angle H(w)) \end{cases}$

$$\text{在 Fourier 分析中 } f(t) = \sum_{n=-\infty}^{\infty} F_n e^{jn\omega_0 t} \rightarrow \text{LTI} \rightarrow y(t) = \sum_{n=-\infty}^{\infty} H(n\omega_0) F_n e^{jn\omega_0 t}$$

或者写为 compact 形式： $f(t) = \frac{C_0}{2} + \sum_{n=1}^{\infty} C_n \cos(n\omega_0 t + \theta_n) \rightarrow \text{LTI} \rightarrow y = H(j) \frac{C_0}{2} + \sum_{n=1}^{\infty} |H(n\omega_0)| C_n \cos(n\omega_0 t + \theta_n + \angle H(n\omega_0))$

$$\text{例: } f(t) = \begin{cases} 1 & t \in [0, 1) \\ 0 & t \in [1, 2) \end{cases} = \frac{1}{2} + \sum_{n=1, \text{odd}}^{\infty} \frac{1}{jn\pi} e^{jnw_0 t}, \quad H(w) = \frac{1.5}{2+jw}, \text{ 求 steady-state output } y(t)$$

$$y(t) = \frac{1}{2} H(0) + \sum_{n=1, \text{odd}}^{\infty} H(nw_0) \cdot \frac{1}{jn\pi} e^{jnw_0 t}$$

Average power and Parseval's theorem

Parseval 指出, $\frac{1}{T} \int_0^T |f(t)|^2 dt = \sum_{n=-\infty}^{\infty} |F_n|^2$, 即时域中 $|f(t)|^2$ 的平均值等于各频谱分量强度 $|F_n|^2$ 的总和

$$f(t) \text{ 也可写成三角形式, 即 } f(t) = \frac{C_0}{2} + \sum_{n=1}^{\infty} C_n \cos(nw_0 t), \text{ 此时有 } \begin{cases} \frac{1}{T} \int_0^T \left(\frac{C_0}{2}\right)^2 dt = \frac{C_0^2}{4} \\ \frac{1}{T} \int_0^T [C_n \cos(nw_0 t)]^2 dt = \frac{C_n^2}{2} \end{cases}$$

rect 函数, 在 $w \in [-\frac{1}{2}, \frac{1}{2}]$ 时
 $\text{rect}(x) = 1$, 其余为 0.

$$\Rightarrow P = \frac{C_0^2}{4} + \sum_{n=1}^{\infty} \frac{C_n^2}{2}$$

$$\text{例: 对于 } f(t) = \begin{cases} 0 & t \in [0, 1) \\ 1 & t \in [1, 2) \end{cases}, \quad H(w) = \boxed{\text{rect}(\frac{w}{8\pi})} \text{ 求 } f(t) \text{ 和稳态输出 } y(t) \text{ 的 average power}$$

$$P_f = \frac{1}{T} \int_T |f(t)|^2 dt = \frac{1}{2} \int_0^1 |1|^2 dt = \frac{1}{2} T$$

$$\text{试用 } P_f = \sum_{n=1, \text{odd}}^{\infty} |F_n|^2 = \frac{1}{4} + \sum_{n=1, \text{odd}}^{\infty} \left| \frac{1}{jn\pi} \right|^2 = \frac{1}{4} + \sum_{n=1}^{\infty} \left(\frac{1}{n\pi} \right)^2$$

对于 $y(t)$, 因为 $w_0 = \pi$, 所以有效的频率只有 $0, \pm\pi, \pm3\pi$

$$\begin{aligned} i.y(t) &= \frac{1}{2} H(0) + \sum_{n=1, \text{odd}}^{\infty} H(nw_0) \frac{1}{jn\pi} e^{jnw_0 t} = \frac{1}{2} + \frac{1}{j\pi} e^{j\pi t} + \frac{1}{j(-3\pi)} e^{-j3\pi t} + \frac{1}{j3\pi} e^{j3\pi t} + \frac{1}{j(-5\pi)} e^{-j5\pi t} \\ &= \frac{1}{2} + \frac{2}{\pi} \sin(\pi t) + \frac{2}{3\pi} \sin(3\pi t) \end{aligned}$$

$$\therefore P_y = \frac{1}{4} + \frac{4}{\pi^2} \times \frac{1}{2} + \frac{4}{9\pi^2} \times \frac{1}{2} = \frac{1}{4} + \frac{20}{9\pi^2}$$

Total Harmonic Distortion (THD)

$$f(t) = \cos(\omega_0 t) \rightarrow \text{non-LTI} \rightarrow y(t) = \frac{C_0}{2} + C_1 \cos(\omega_0 t) + C_2 \cos(2\omega_0 t) + \dots$$

$$\text{THD} = \frac{\text{power in harmonics}}{\text{power in } w_0} = \frac{\frac{C_1^2}{2} + \frac{C_2^2}{4} + \dots}{\frac{C_0^2}{2}} = \frac{P_y - \frac{C_0^2}{4} - \frac{C_1^2}{2}}{\frac{C_1^2}{2}}$$

例 : $f(t) = \sin(\pi t) \rightarrow \text{non-LTI} \rightarrow y(t) = \begin{cases} 1 & t \in [0, 1] \\ -1 & t \in [1, 2] \end{cases} = \frac{4}{\pi} \left[\cos(\pi t - \frac{\pi}{2}) + \frac{1}{3} \cos(3\pi t - \frac{\pi}{2}) + \dots \right]$

算 THD

$$\text{THD} = \frac{P_y - \frac{C_0^2}{4} - \frac{C_2^2}{2}}{\frac{C_0^2}{2}} = \frac{\pi^2 - 8}{8} \approx 0.23$$